

1. Quiz for Chapter 2&3


1) The gate input cost G of function $F = AB(C + D) + C(\overline{BD} + \overline{AD})$ is ____.

- A. 15 B. 14 C. 13 D. 12


answer: A.

2) The Essential Prime Implicants in the K-Map given below are ____.

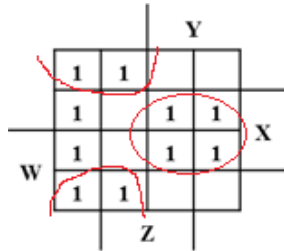- A. $Y'Z'$, XZ' B. $X'Y'$, XY C. XY , XZ' D. $Y'Z'$, $X'Y'$




answer: B.

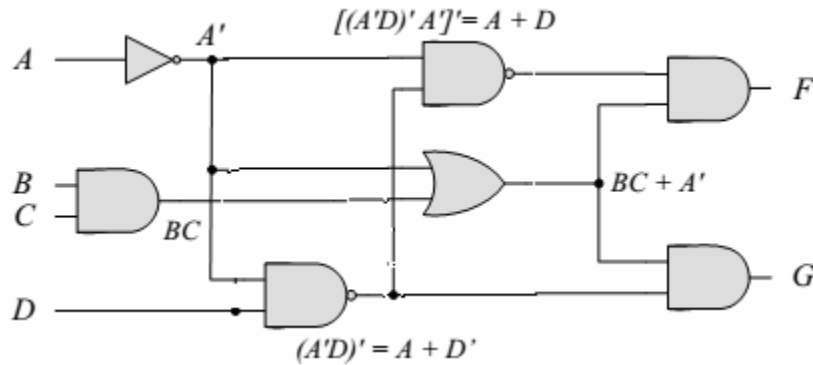

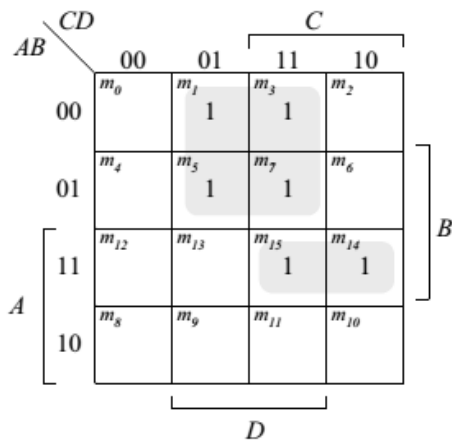
3) Obtain the simplified Boolean expressions for output F in terms of the input variables for the above logic circuit diagram.

$$F = (A + D)(A' + BC) = A'D + ABC + BCD + A'D + ABC$$

$$F = (A + D')(A' + BC) = A'D' + ABC + BCD' = A'D' + ABC$$



$$F = A'D + ABC + BCD = A'D + ABC$$

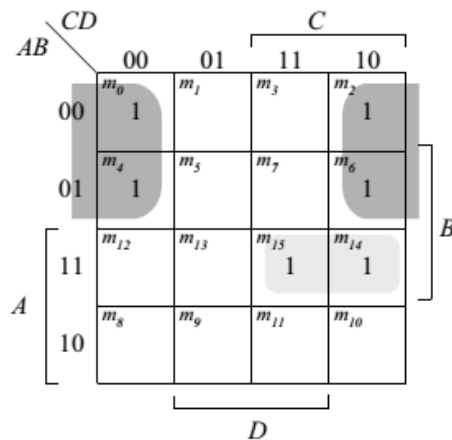

$$G = A'D' + ABC + BCD' = A'D' + ABC$$

- 4) Optimize the following Boolean functions F together with the don't-care conditions: $F(A, B, C, D) = \sum_m(0, 1, 7, 13, 15) + \sum_d(2, 6, 8, 9, 10)$

AB \ CD	00	01	11	10
00	1	1		x
01			1	x
11		1	1	
10	x	x		x

$$F = \overline{\overline{B}}\overline{\overline{C}} + ABD + BCD$$